

# Resource Sharing in Stratix IV

Stefan Hadjis  
August 25<sup>th</sup> 2011

# Binding in High Level Synthesis

- Binding reduces circuit area by sharing functional units among multiple inputs
- Intuitively it makes sense to share larger operations or chains of smaller operations


# Binding in High Level Synthesis

- Binding reduces circuit area by sharing functional units among multiple inputs
- Intuitively it makes sense to share larger operations or chains of smaller operations

## Original LegUp Release

- In Cyclone II Architecture, sharing is beneficial for **dividers** and **remainders** (mod), which are large operations
- E.g. if a circuit needs to perform division 10 times, it is cheapest to have one divider with 10-to-1 muxing on its inputs






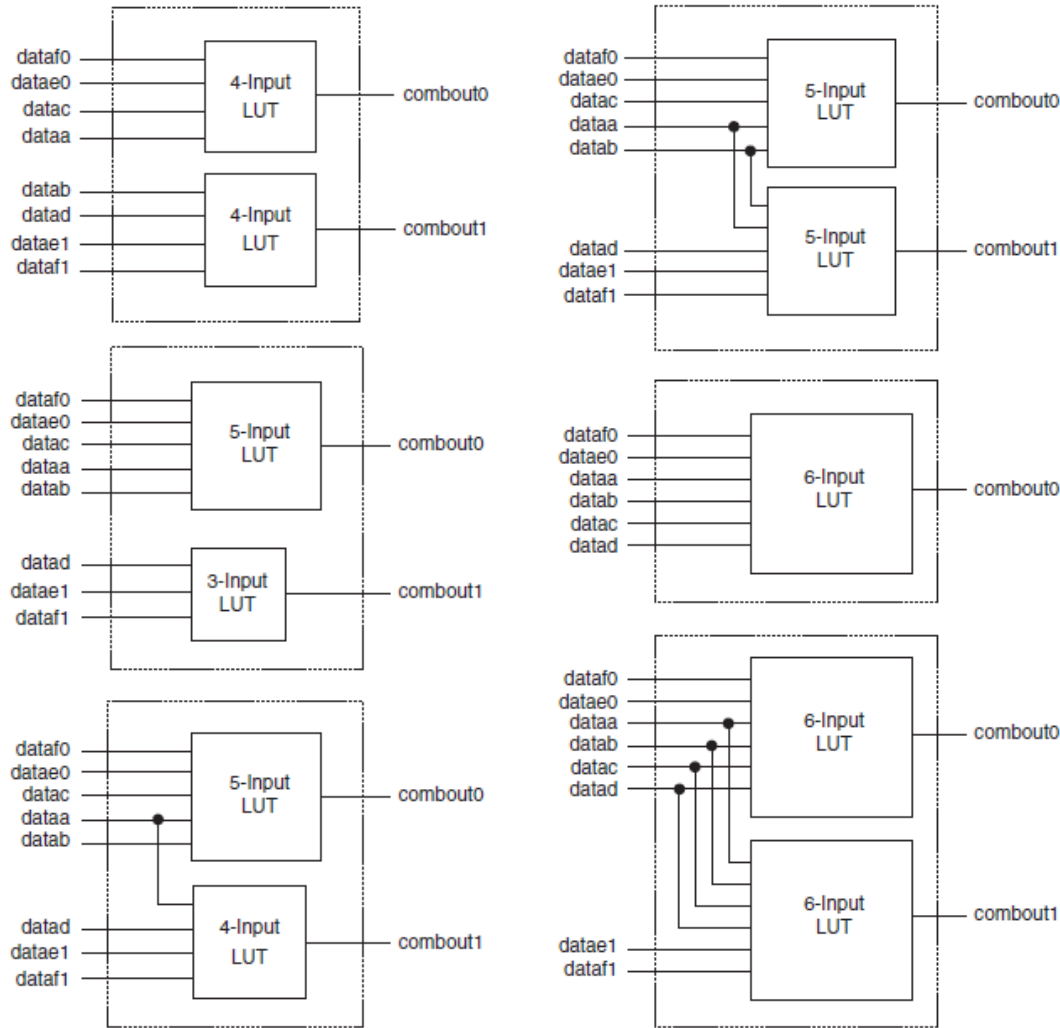
# Stratix IV, Adaptive Logic Modules (ALM)



Each ALM contains 2 Adaptive LUTs (ALUTs) which can implement a function of between 4 and 7 inputs

# Stratix IV, Adaptive Logic Modules (ALM)

Cyclone II

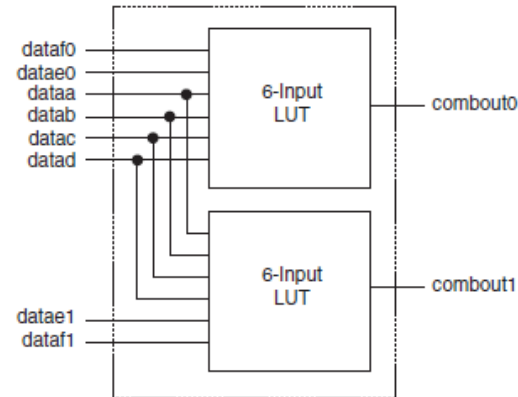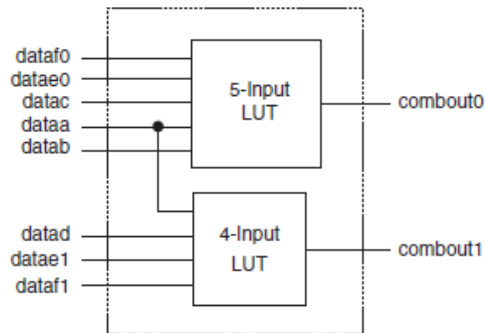 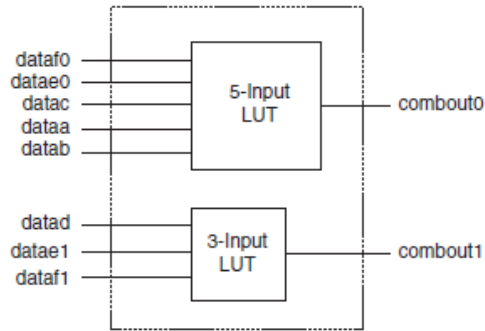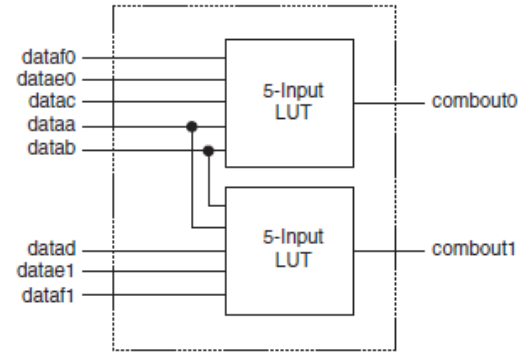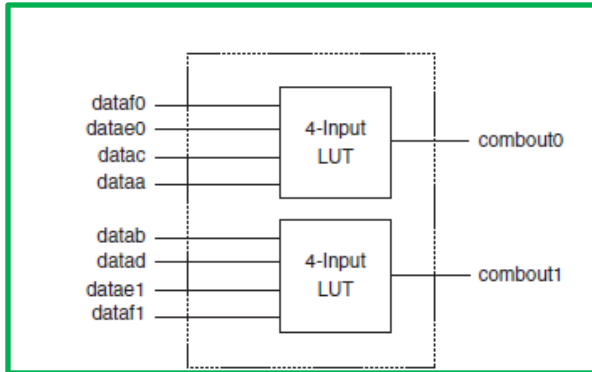

Each ALM contains 2 Adaptive LUTs (ALUTs) which can implement a function of between 4 and 7 inputs


# Binding in Stratix IV

- All of the circuits created by LegUp tend to use mostly 2 and 3 input functions (LUTs)
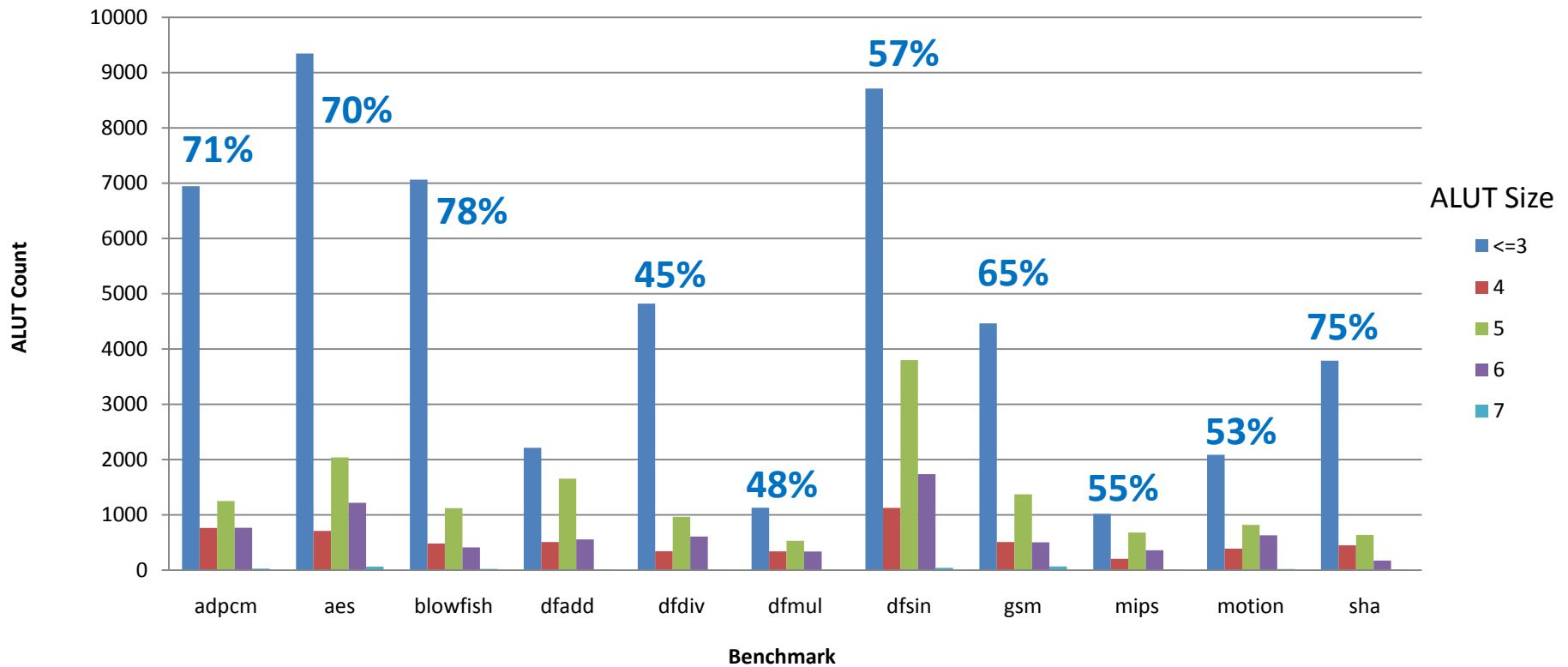
# Binding in Stratix IV

- All of the circuits created by LegUp tend to use mostly 2 and 3 input functions (LUTs)

Proportion of ALUT Sizes for the CHStone Benchmarks



Average: 62%

# Binding in Stratix IV

- All of the circuits created by LegUp tend to use mostly 2 and 3 input functions (LUTs)
- For example, a bitwise AND of two 32-bit numbers requires 32 ALUTs, but each is only size 2 (2 input bits, 1 output bit)




# ALM Example

- Consider two circuits:

**Circuit 1:** Implemented using 100 **3-input LUTs**







**Circuit 2:** Implemented using 45 **3-input LUTs** and 45 **5-input LUTs**

# Adaptive Logic Modules (ALM)

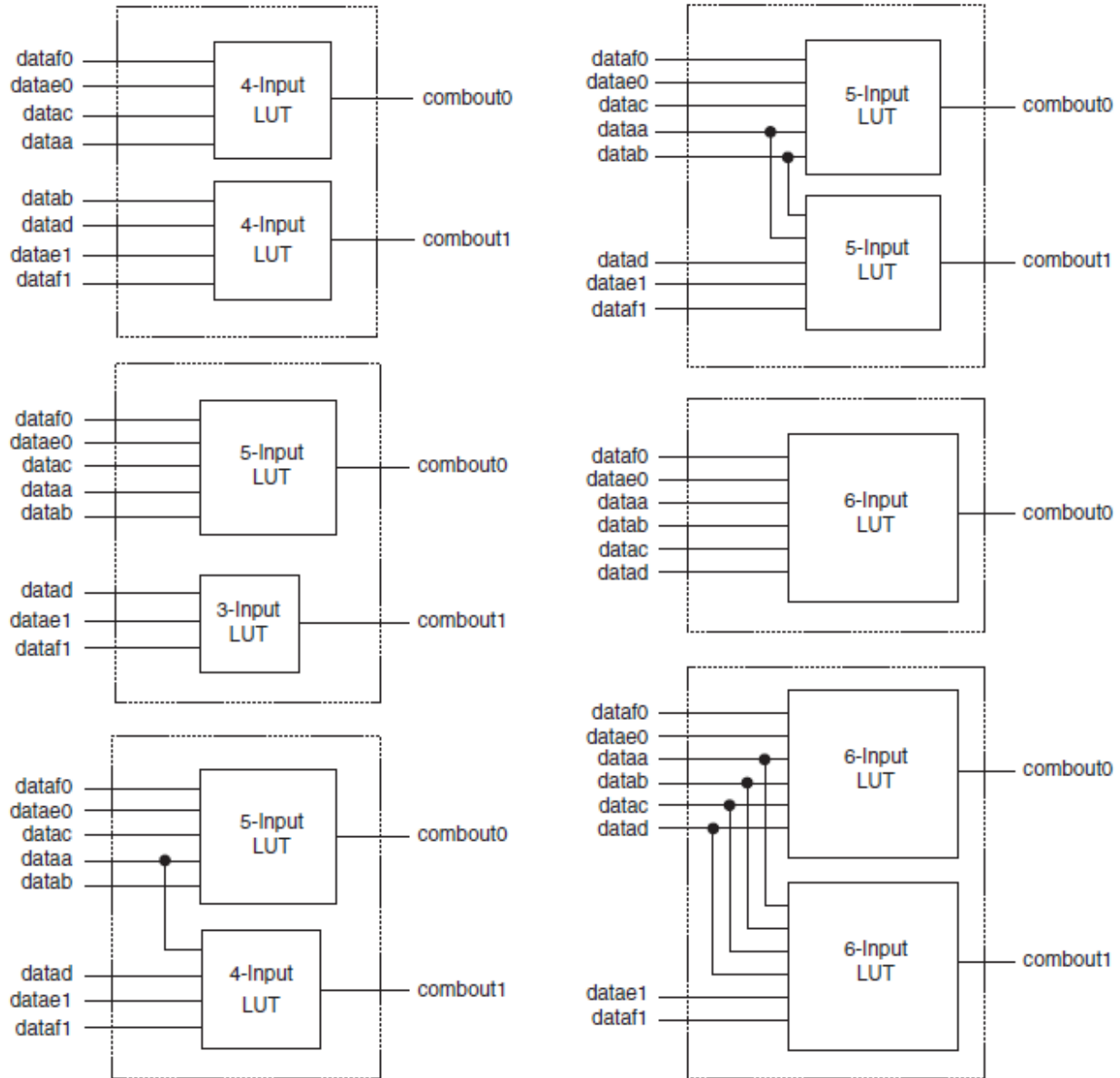


# Adaptive Logic Modules (ALM)

50

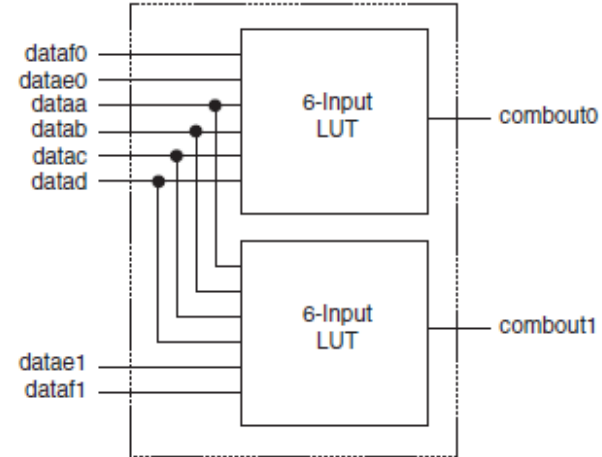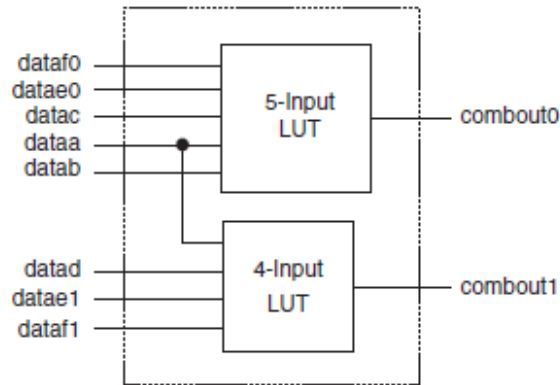
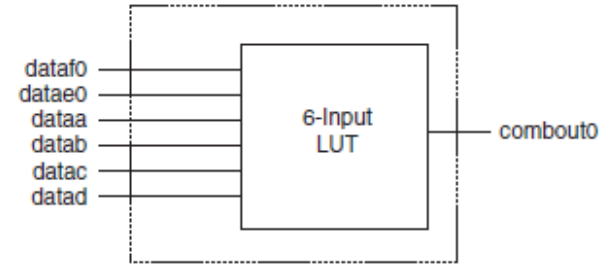
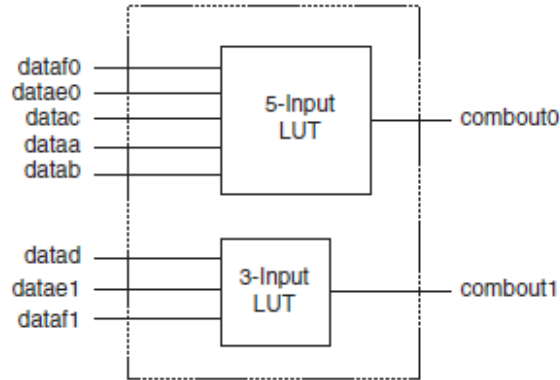
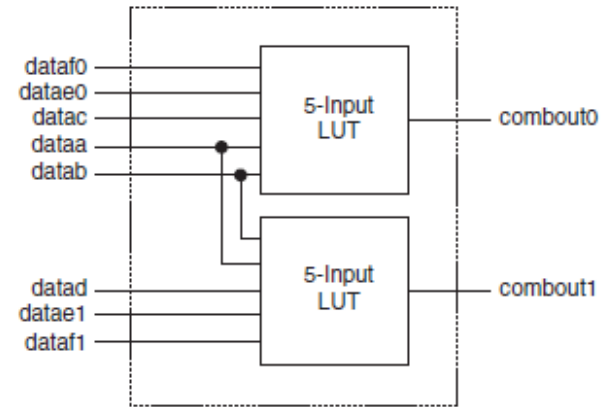
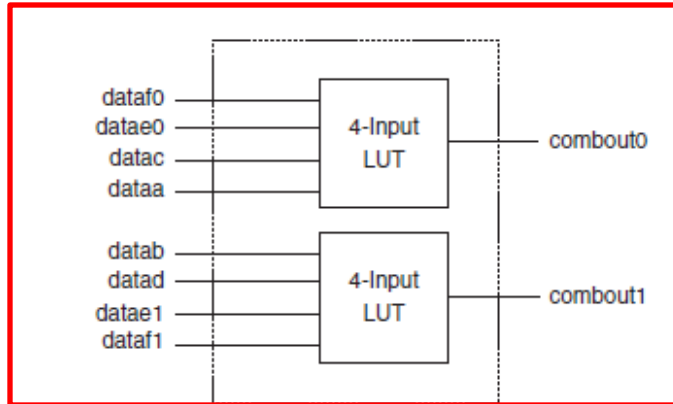


# Adaptive Logic Modules (ALM)

50

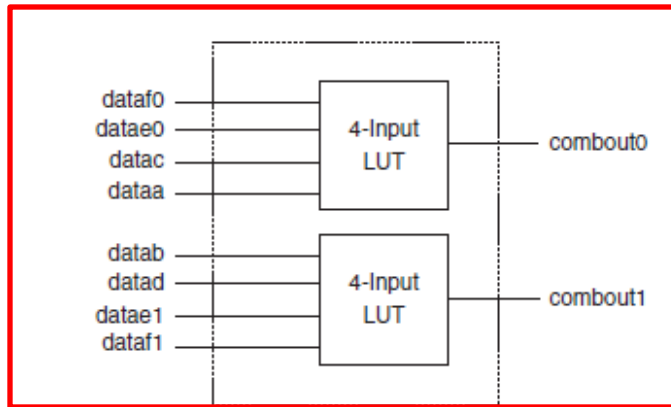

45

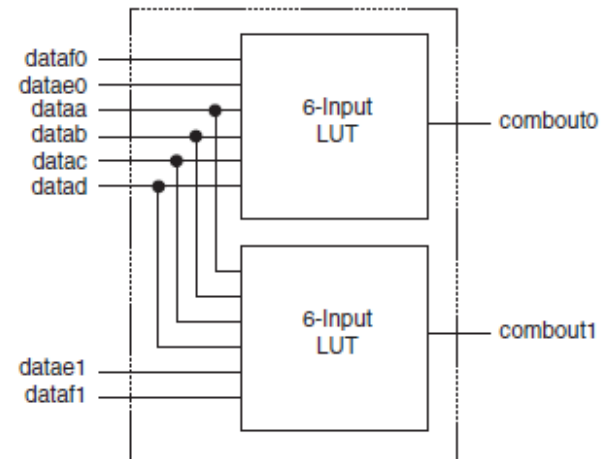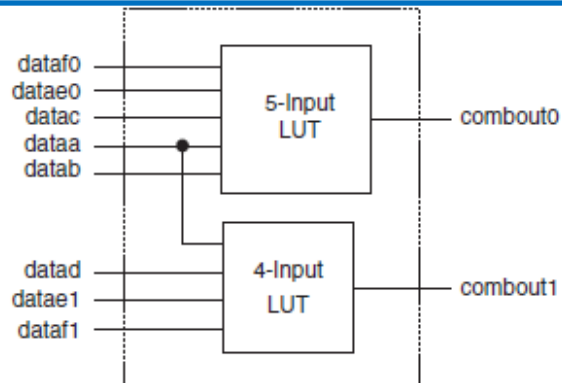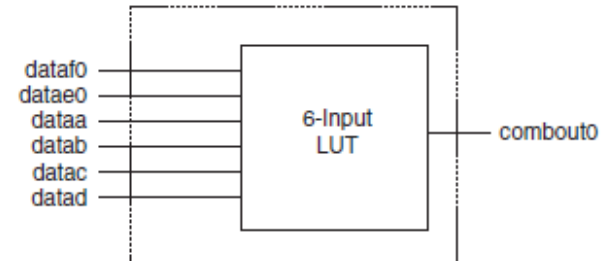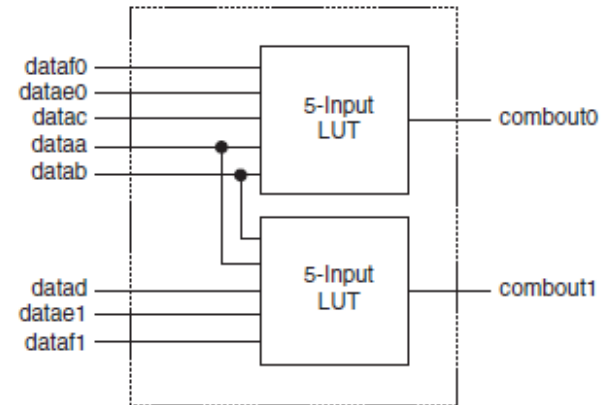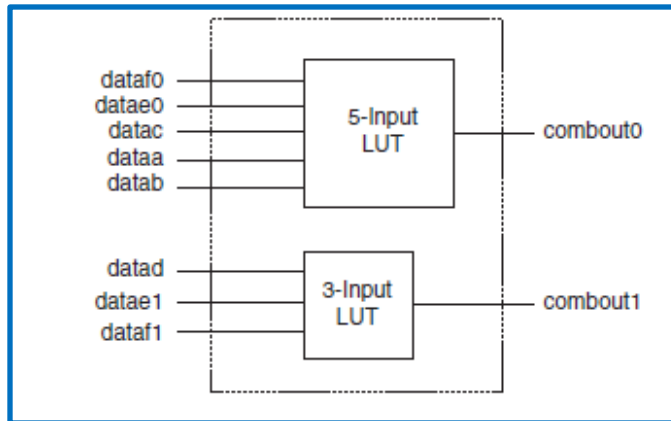

# ALM Example

- Consider two circuits:

**Circuit 1:** Implemented using 100 **3-input LUTs**

**Circuit 2:** Implemented using 45 **3-input LUTs** and 45 **5-input LUTs**

# ALM Example

- Consider two circuits:

**Circuit 1:** Implemented using 100 **3-input LUTs**

→ Requires **50 ALMs**

**Circuit 2:** Implemented using 45 **3-input LUTs** and 45 **5-input LUTs**

# ALM Example

- Consider two circuits:

**Circuit 1:** Implemented using 100 **3-input LUTs**

→ Requires **50** ALMs

**Circuit 2:** Implemented using 45 **3-input LUTs** and 45 **5-input LUTs**

→ Requires **45** ALMs, even though the circuit contains more logic

# Sharing Single Operations

- Given that LegUp-generated circuits contain mostly 2-3 input functions therefore, the number of ALMs can be reduced by packing many “smaller LUTs” into fewer “larger LUTs”




## Example – Sharing Bitwise Operations

- A 1-bit **2-to-1 multiplexor** requires a 3-input LUT (2 inputs and select), whereas a 1-bit **Bitwise AND** requires only a 2-input LUT

 
## Example – Sharing Bitwise Operations

- A 1-bit **2-to-1 multiplexor** requires a 3-input LUT (2 inputs and select), whereas a 1-bit **Bitwise AND** requires only a 2-input LUT
- Intuitively therefore, it does not make sense to do this:




## Example – Sharing Bitwise Operations

- A 1-bit **2-to-1 multiplexor** requires a 3-input LUT (2 inputs and select), whereas a 1-bit **Bitwise AND** requires only a 2-input LUT
- Intuitively therefore, it does not make sense to do this:

 

Two 2-input LUTs

 

One 5-input LUT

## Example – Sharing Bitwise Operations

- A 1-bit **2-to-1 multiplexor** requires a 3-input LUT (2 inputs and select), whereas a 1-bit **Bitwise AND** requires only a 2-input LUT
- However, sharing a bitwise operation uses half the LUTs – one 5-input LUT versus two 2-input LUTs
- If the circuits therefore contain many more small LUTs than large LUTs, sharing bitwise operations reduces ALMs


## Example – Sharing Bitwise Operations

- A 1-bit **2-to-1 multiplexor** requires a 3-input LUT (2 inputs and select), whereas a 1-bit **Bitwise AND** requires only a 2-input LUT
- However, sharing a bitwise operation uses half the LUTs – one 5-input LUT versus two 2-input LUTs
- If the circuits therefore contain many more small LUTs than large LUTs, sharing bitwise operations reduces ALMs
- Therefore, sharing even small operations reduces ALUT and ALM usage

# Live Variable Analysis

- Next, if the output of each shared operation was originally connected to a register, then using **Live Variable Analysis**, operations whose live intervals do not overlap can be shared to save registers

# Live Variable Analysis

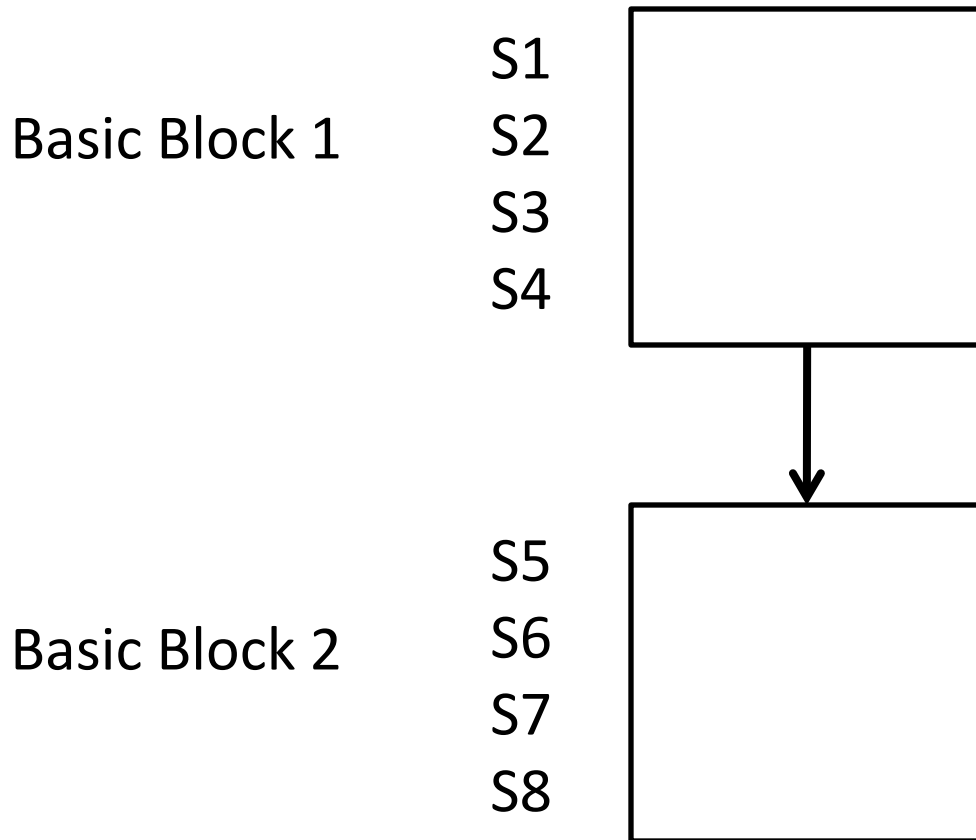

# Live Variable Analysis

Basic Block 1

S1

S2

S3

S4

%a = ...

...= %a + ...



Basic Block 2

S5

S6

S7


S8

%b = ...


...= %b + ...



# Live Variable Analysis

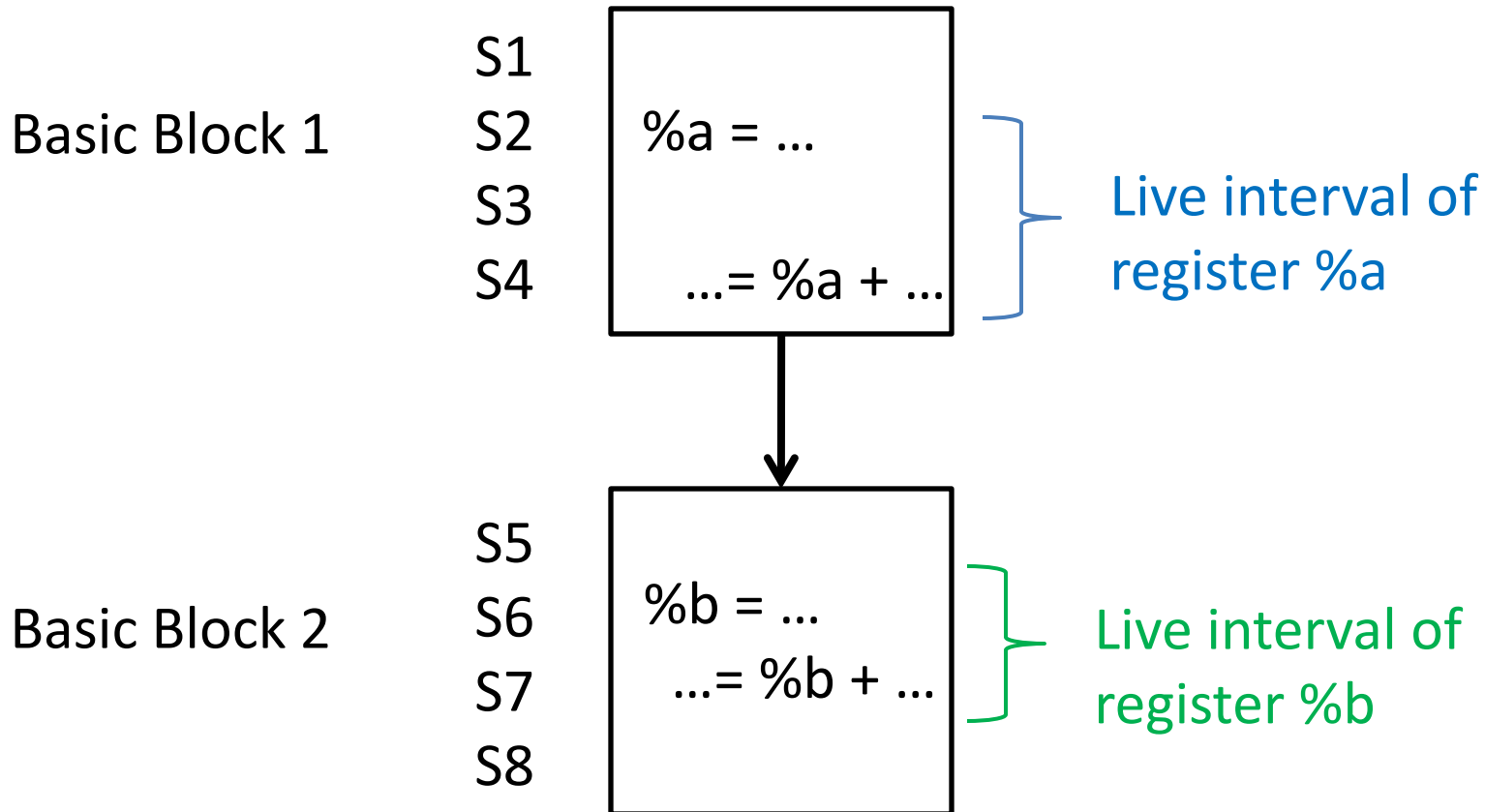

# Live Variable Analysis

 

E.g. for a 32-bit add, save 32 registers

# Live Variable Analysis


- Created an LLVM pass which calculates post-scheduling liveness information for each register
- Used to map every instruction to a set of other instructions with which it is independent
- This represents a graph, where nodes are instructions and edges represent independence
- Common instructions (e.g. all adders) are then paired and pairs are shared to save registers

# Altera Resource Sharing

- Quartus II has a Resource Sharing synthesis option
- Shares adders, subtractors and multipliers
- However, none of the circuits tested were affected by this option

 
# Sharing Chains of Operations

- So far, ALUTs and Registers were saved by sharing single operations
- Consider:



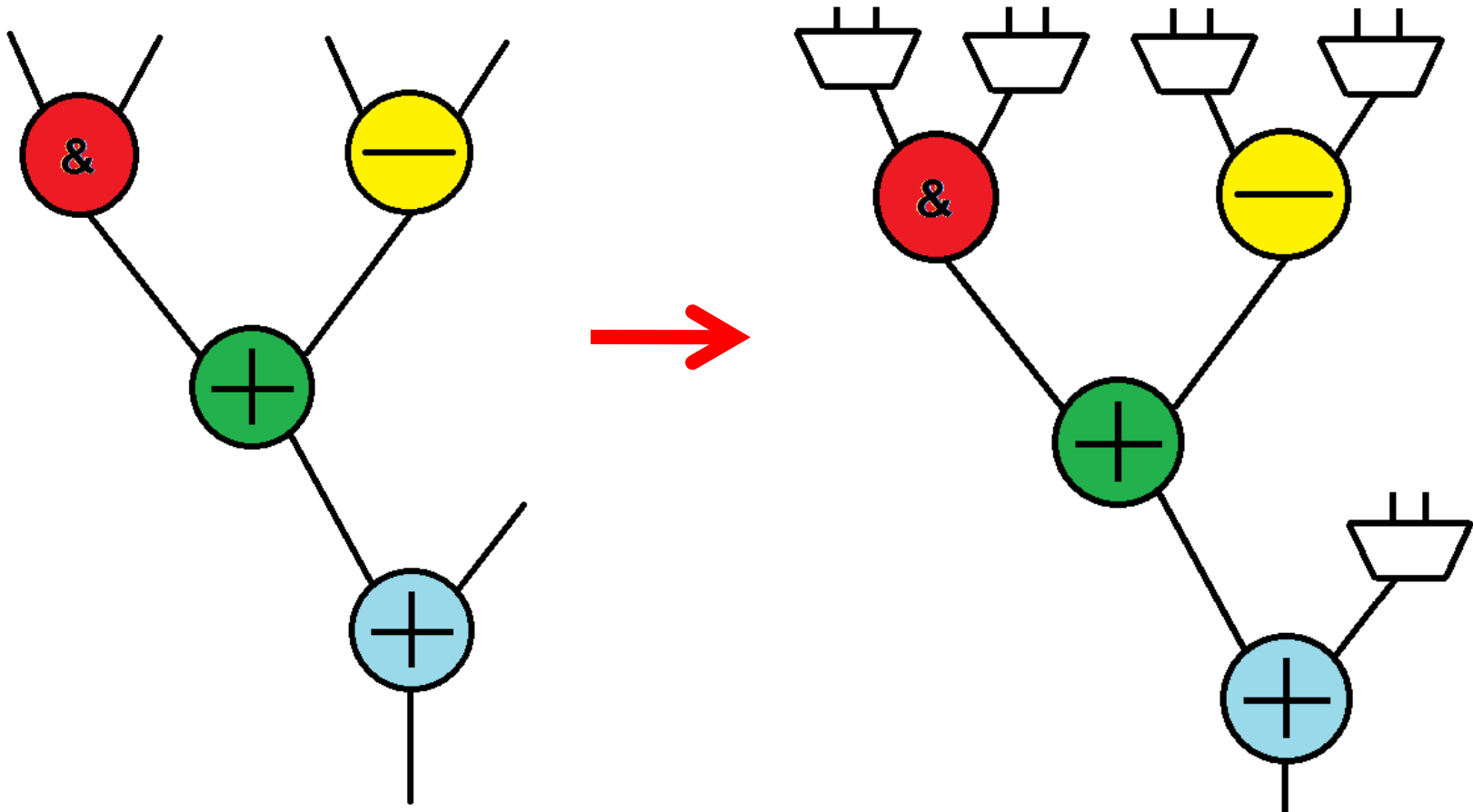
# Sharing Chains of Operations

- So far, ALUTs and Registers were saved by sharing single operations
- Consider:



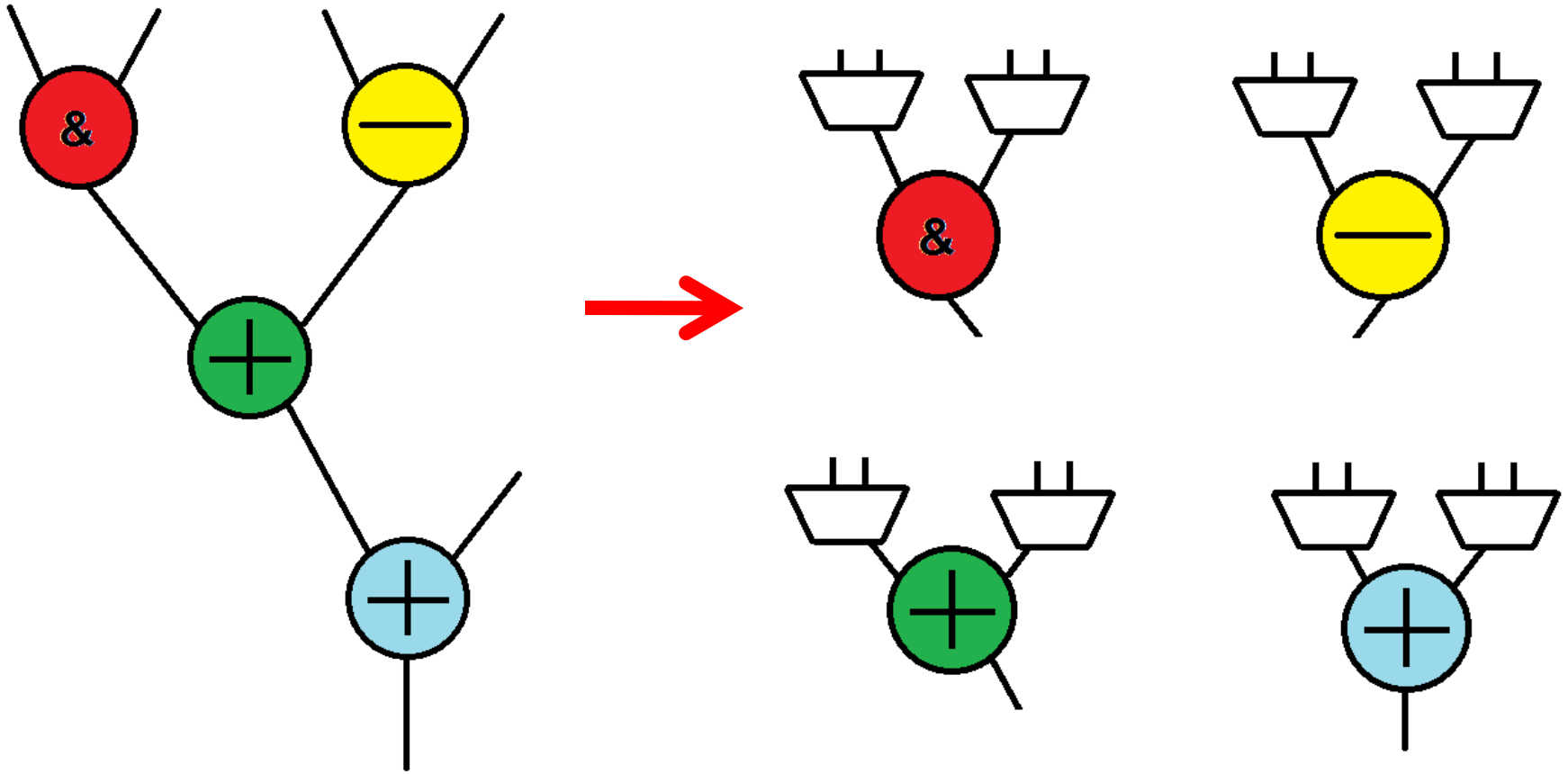
# Sharing Chains of Operations

- So far, ALUTs and Registers were saved by sharing single operations
- Consider:


 
# Sharing Chains of Operations


- So far, ALUTs and Registers were saved by sharing single operations
- Consider:





 
# Sharing Chains of Operations

- So far, ALUTs and Registers were saved by sharing single operations
- Consider:


 
# Sharing Chains of Operations

- So far, ALUTs and Registers were saved by sharing single operations
- Consider:



# Sharing Chains of Operations

- So far, ALUTs and Registers were saved by sharing single operations
- By sharing chains instead of only single operations, the amount of multiplexing is reduced and ALUTs decrease further

# Sharing Chains of Operations


- So far, ALUTs and Registers were saved by sharing single operations
- By sharing chains instead of only single operations, the amount of multiplexing is reduced and ALUTs decrease further
- Intuitively, as larger patterns are considered, their frequency of occurrence will decrease

# Sharing Chains of Operations

- So far, ALUTs and Registers were saved by sharing single operations
- By sharing chains instead of only single operations, the amount of multiplexing is reduced and ALUTs decrease further
- Intuitively, as larger patterns are considered, their frequency of occurrence will decrease
- Therefore, an iterative algorithm is used to find patterns of all sizes
 
# Sharing Chains of Operations

- Computational patterns are represented as **Directed Graphs**, with a single output (“root”) node:



- Graph traversal algorithms are then used to compare graphs and group together similar patterns for sharing

# Sharing Algorithm

**S1**


**S2**

**S3**

**S4**




# Sharing Algorithm

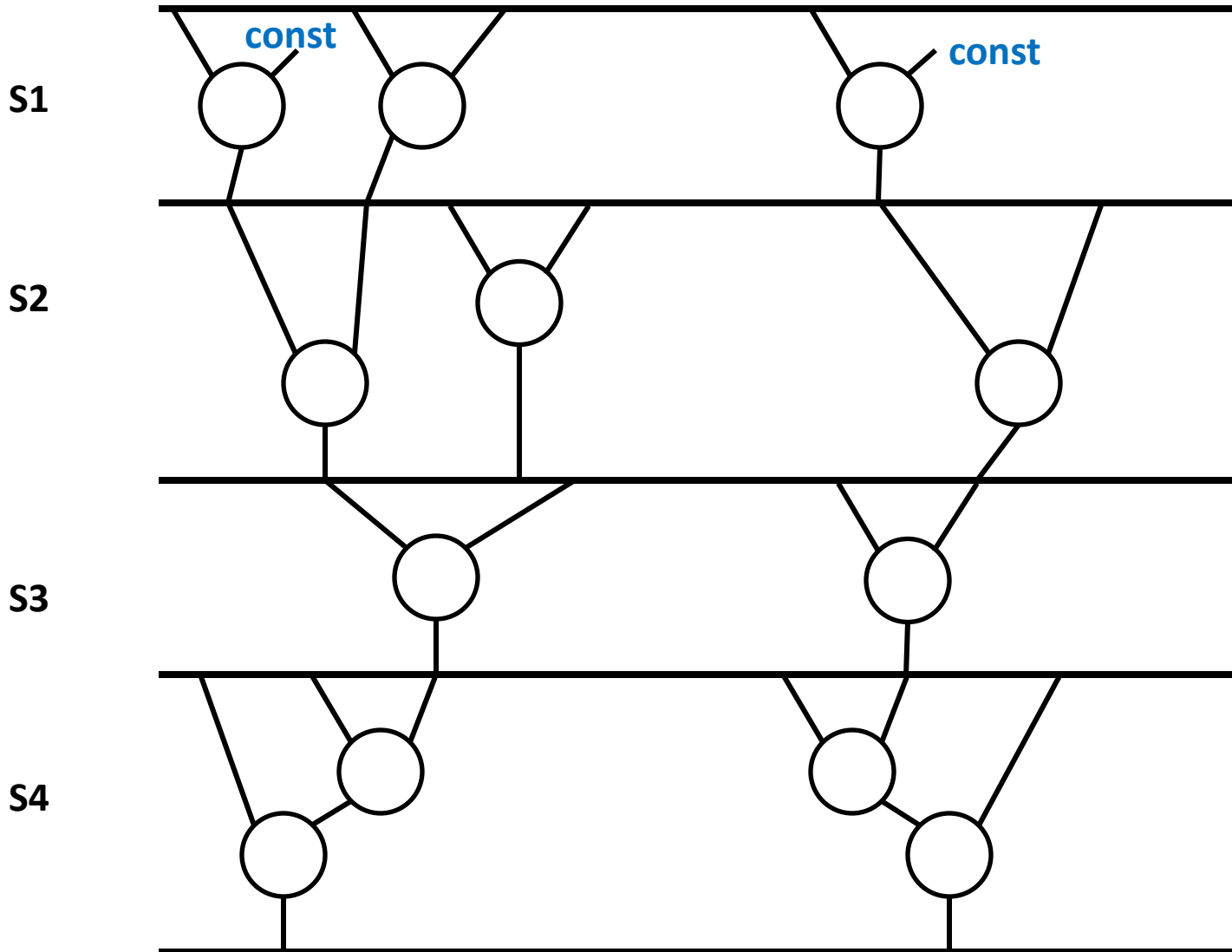





# Sharing Algorithm

 


# Sharing Algorithm

 


# Sharing Algorithm

 


# Sharing Algorithm

 


# Sharing Algorithm

 


# Sharing Algorithm

 

# Sharing Algorithm

 


# Sharing Algorithm

 





# Sharing Algorithm

 


# Sharing Algorithm

 


# Sharing Algorithm

 


# Sharing Algorithm

 


# Sharing Algorithm

 


# Sharing Algorithm

 

# Sharing Algorithm

 


# Sharing Algorithm

 




# Sharing Algorithm

 

# Sharing Algorithm


Number of Graphs found: 3

 


# Sharing Algorithm

- The animation illustrates how graphs are found
- However, the three graphs all occurred with frequency 1 and hence no sharing could take place


# Sharing Algorithm

 


# Sharing Algorithm

 


# Sharing Algorithm

 

# Sharing Algorithm

 


# Sharing Algorithm

 





# Sharing Algorithm

 


# Sharing Algorithm

 


# Sharing Algorithm

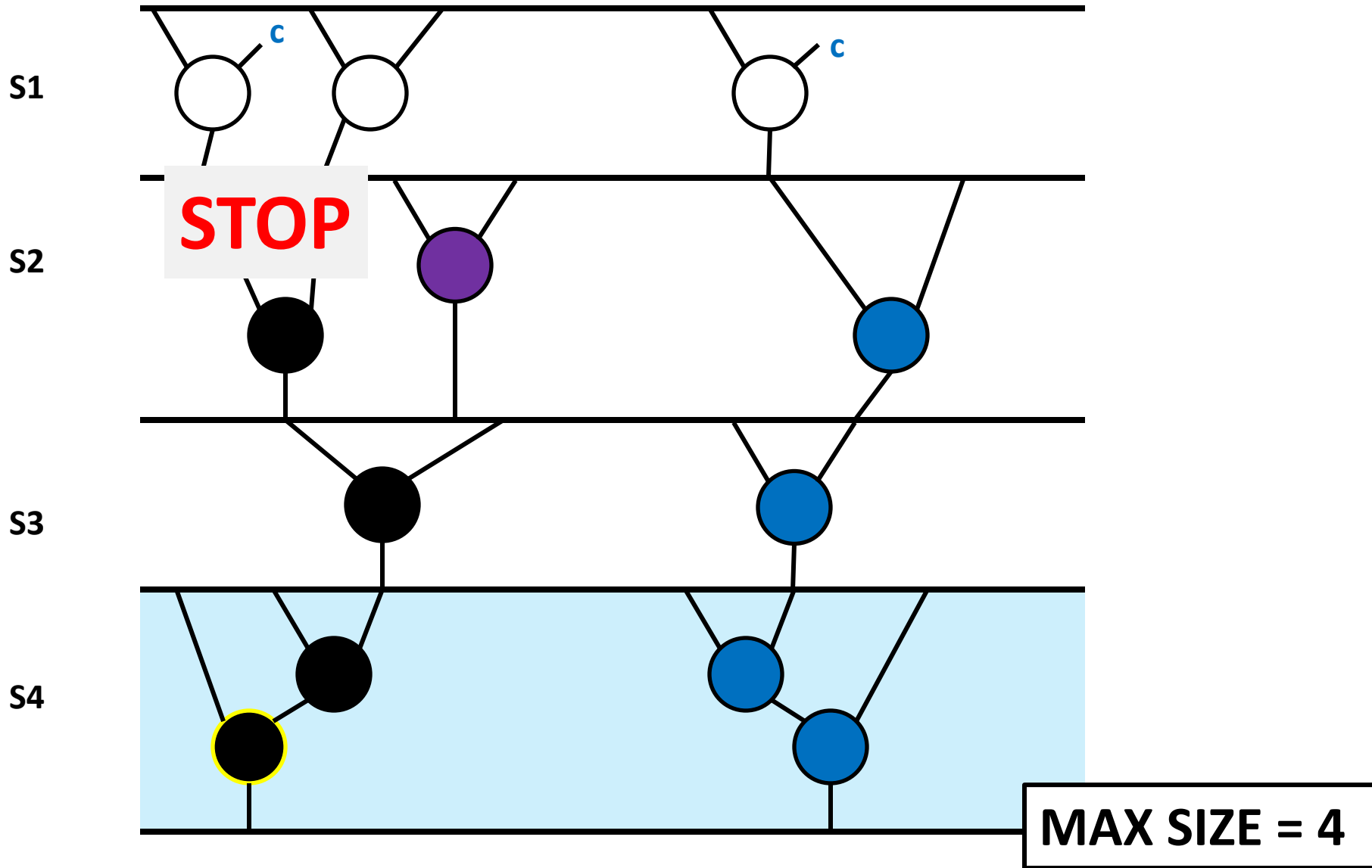


# Sharing Algorithm

 

# Sharing Algorithm

 

# Sharing Algorithm

 


# Sharing Algorithm

- These graphs still can't be shared however because their live intervals overlap, therefore this is the last check in the algorithm
- Graphs are then shared in LegUp Binding.cpp

# Results




## ALMs

 


**Average: 3.2%**

## ALMs

 


**Average: 3.2%**

## ALUTs

 


**Average: 6.5%**
 
## Proportion of ALUT Sizes for CHStone Benchmarks (Sharing)




**Average: 45%**  
**(was 62%)**

# Registers

 


**Average: 4.9%**

# Fmax

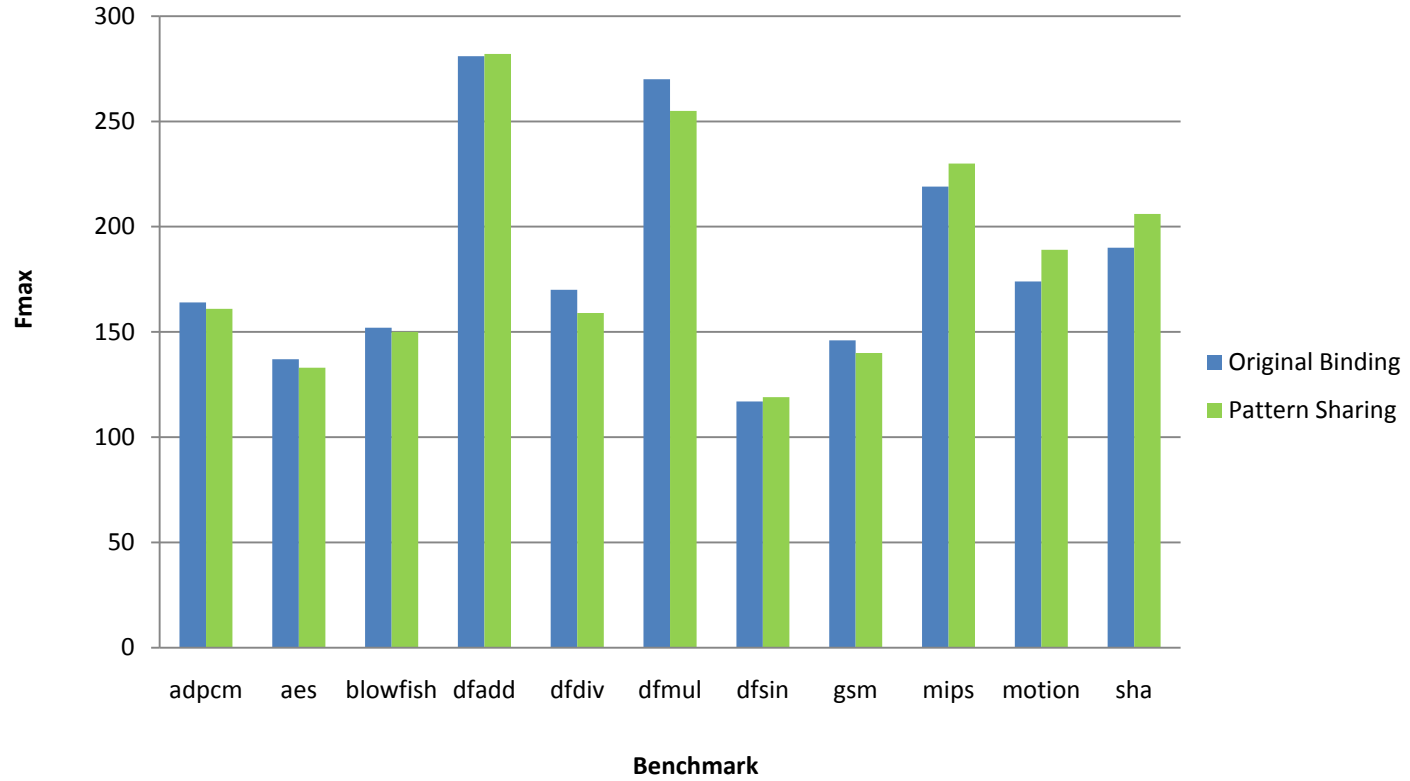


## ALMs

 

**Average: 3.2%**


## ALMs

 

**Average: 3.9%**




# ALMs

 


**Average: 4.0%**

Current Work – Intelligently Pairing Patterns


# Current Work

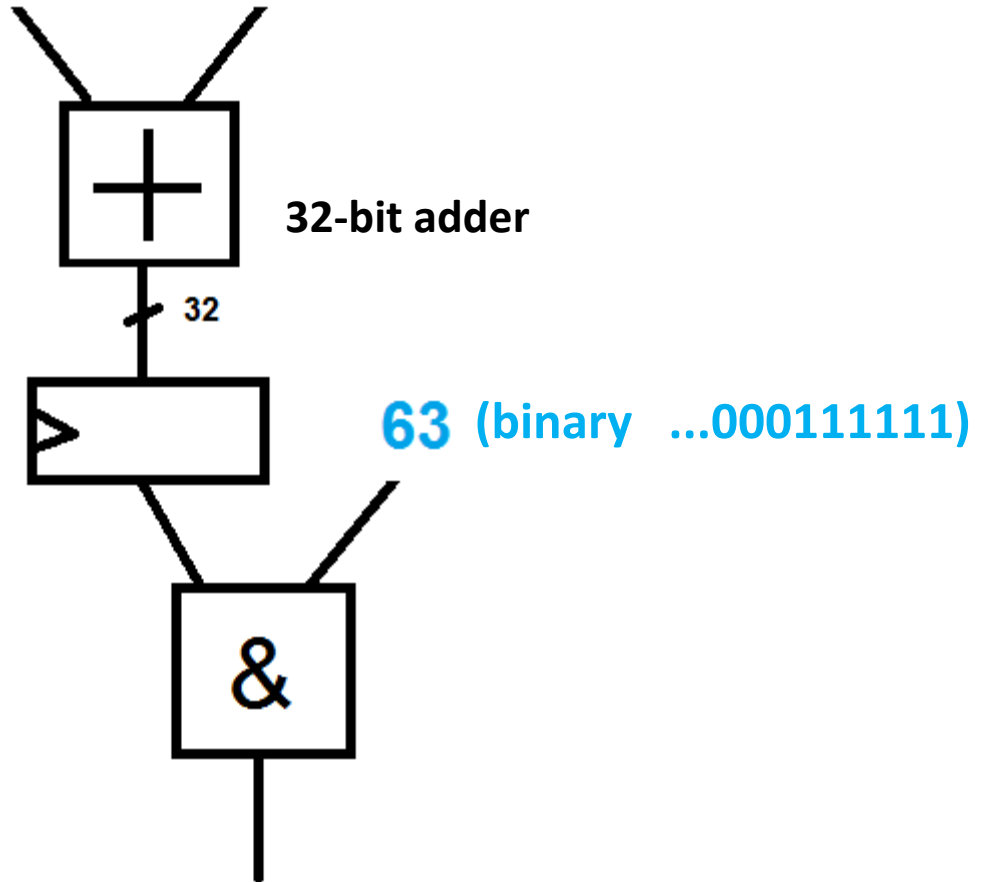




# Current Work

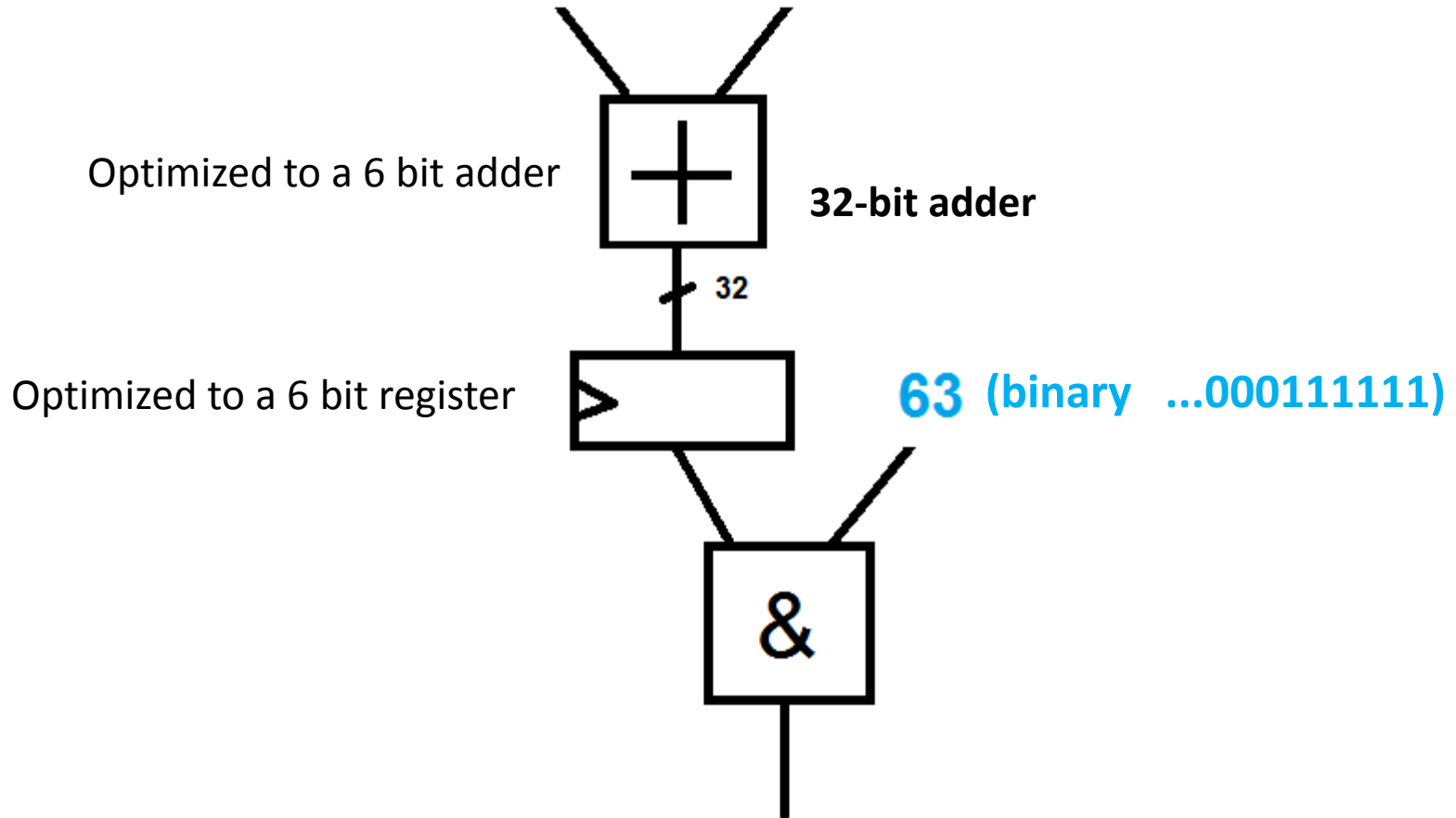




# Current Work

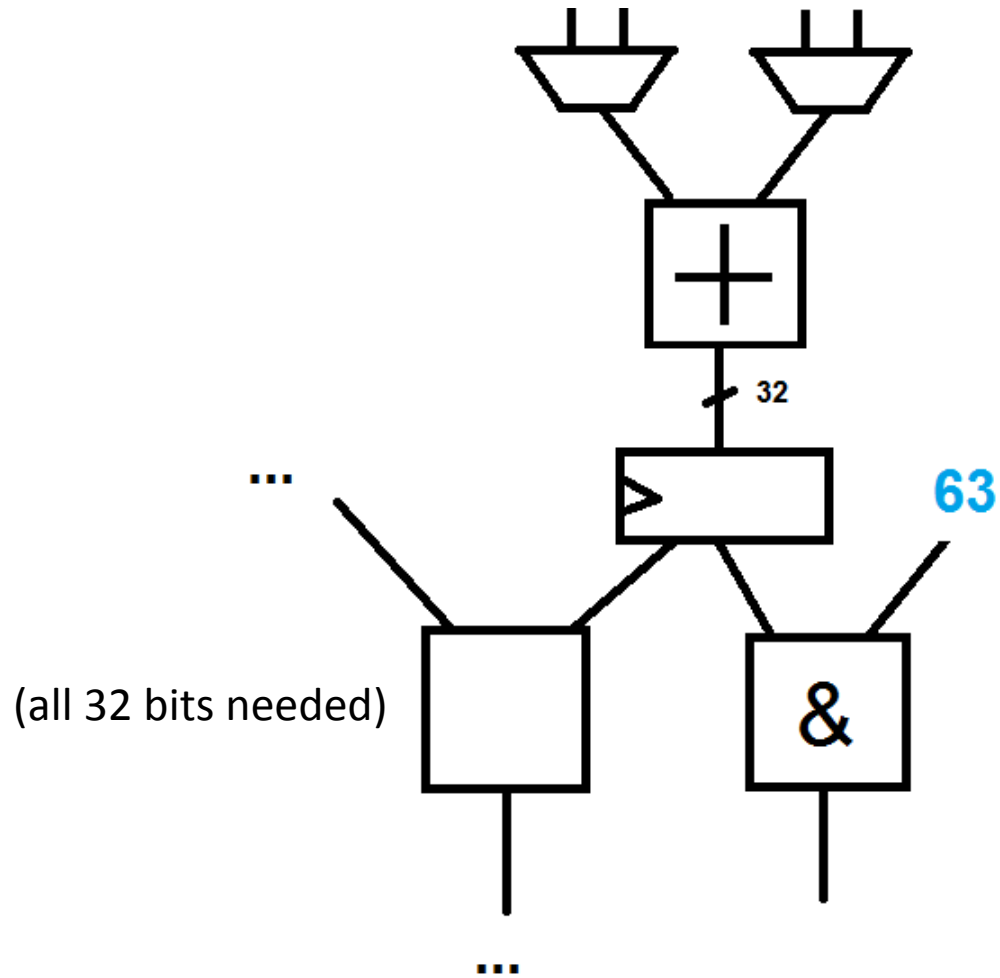

# Current Work

 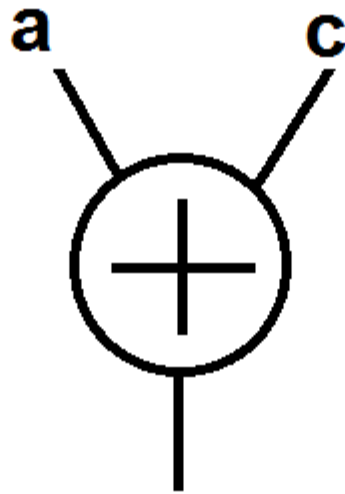 

# Current Work

 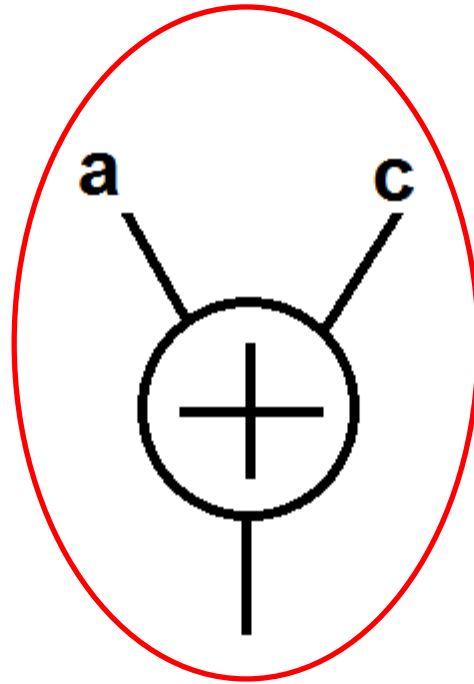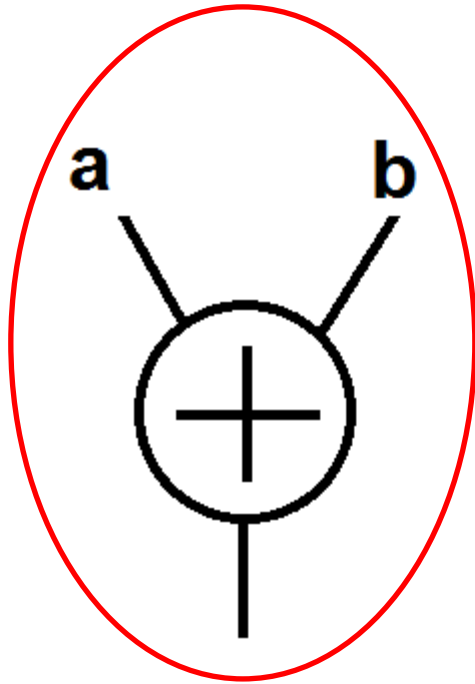

# Current Work

